

Computer Systems

Lecture 4

Boolean Algebra and Arithmetic

Dr José Cano, Dr Lito Michala

School of Computing Science

University of Glasgow

Spring 2020

Outline

- Boolean algebra
- Addition and subtraction
 - Half adder
 - Full adder
 - Ripple carry adder
 - Subtraction
- Circuit simulation

Boolean algebra

- Elementary algebra is about properties of operations on numbers: $+$ $-$ \times \div
 - **Example:** $x + y = y + x$
 - Elementary algebra helps you solve many problems involving numbers
- There are many different algebras, for different kinds of object
- Boolean algebra is about the operations on truth values: 0 and 1
 - **Example:** $x \vee y = y \wedge x$
 - Boolean algebra helps you solve many problems involving truth values

Why learn about Boolean algebra?

- We will use it just a little, not very much
- But you will encounter it again and again in computer science, so a brief introduction helps!
- Boolean algebra makes it easier to understand tricky logic
 - In digital circuits
 - In programming with conditionals
- It's also important in the history and philosophy of mathematics

Constants and operations of Boolean algebra

- There are two values: 0, 1
- We can use variables to stand for a value: x, y, z, ...
- There are three operators
- Each operator corresponds exactly to a logic gate
- Boolean algebra describes the values of signals in a digital circuit
- There is also another operator, logical implication, but it can be expressed using the others

Algebra	Name	Circuit
$\neg x$	not	inv x
$x \vee y$	or	or2 x y
$x \wedge y$	and	and2 x y

Definition of the operations

x	$\neg x$
0	1
1	0

x	y	$x \wedge y$	$x \vee y$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

- These are the same as the definitions of the logic gates
 - Except we don't have a Boolean operator for the “exclusive or” gate

Laws of Boolean algebra

- The basic rules describing logical operations
- Called laws, axioms, rules (what you call them isn't important)
- You can use these to reason about circuits
 - Simplify expressions
 - Calculate signal values
 - Prove that two circuits calculate the same value
 - Derive circuits to meet a specification
- For this course: **don't memorise the laws** (shown on the next slides), but do **know the truth tables for the logic gates**

Operations with constants

- You can verify these using the truth tables for the operations

$$x \wedge 0 = 0$$

$$x \wedge 1 = x$$

$$x \vee 0 = x$$

$$x \vee 1 = 1$$

- These help to work out the values of signals in a circuit

Idempotence

- In general, an operation is idempotent if doing it several times is the same as doing it once
 - On some web sites, registering twice is the same as registering once: here, registration is idempotent
 - But on some other web sites, if you register three times it gives you three separate accounts: here, registration is not idempotent
- Here's the mathematical definition

$$x \vee x = x$$

$$x \wedge x = x$$

- It's straightforward to check these with truth tables
 - Check that they hold for both cases: when $x=0$ and when $x=1$

Commutativity

- Very important!
- These say that you can swap around the order of inputs to an and-gate or an or-gate without changing the result

$$x \vee y = y \vee x$$

$$x \wedge y = y \wedge x$$

Associativity

- These give a way to compute the logical and/or of many inputs, by using several 2-input and/or gates

$$x \vee (y \vee z) = (x \vee y) \vee z$$

$$x \wedge (y \wedge z) = (x \wedge y) \wedge z$$

- These laws are extremely important in advanced computer science
 - High performance circuit design
 - Programming massively parallel high performance computers

Distributive and absorption laws

- Useful in proving correctness of circuits, but we won't need them in this course

$$x \wedge (y \vee z) = (x \wedge y) \vee (x \wedge z)$$

$$x \vee (y \wedge z) = (x \vee y) \wedge (x \vee z)$$

$$x \wedge (x \vee y) = x$$

$$x \vee (x \wedge y) = x$$

Logical reasoning

- We want to be able to work out the consequences of assumptions
- Work with unambiguous statements that are either true or false
- Typical problem: show that two Boolean expressions always have the same value
- One approach: use truth tables
 - But a truth table with n variables contains 2^n lines
- Often it's easier to carry out a calculation using Boolean algebra


Example: equational reasoning

- **Equational reasoning** means “substituting equals for equals” using the laws of algebra
- **Problem:** Use Boolean algebra to simplify $(0 \wedge P) \vee Q$
- Each of these steps uses one of the laws

$$\begin{aligned} & (0 \wedge P) \vee Q \\ &= (P \wedge 0) \vee Q && \wedge \text{ is commutative} \\ &= 0 \vee Q && \text{constant operation on } \wedge \\ &= Q \vee 0 && \vee \text{ is commutative} \\ &= Q && \text{constant operation on } \vee \end{aligned}$$

- For large and complicated calculations, it is easier to use the laws carefully
 - It helps to prevent mistakes

George Boole, 1815-1864

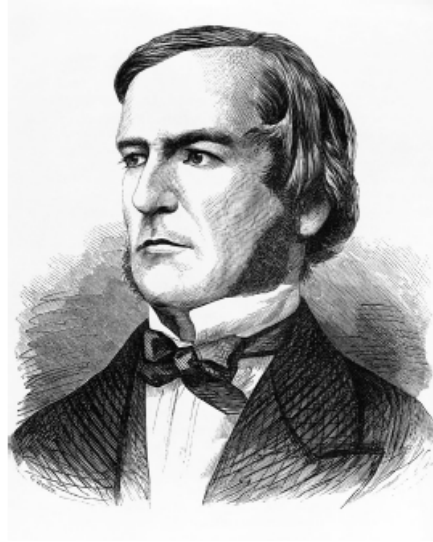

- English mathematician and logician
- Applied algebra to logic
- **Symbolic logic**: formal reasoning instead of arguments in natural language

Outline

- Boolean algebra
- Addition and subtraction
 - Half adder
 - Full adder
 - Ripple carry adder
 - Subtraction
- Circuit simulation

Addition and subtraction

- Addition, subtraction, and negation are all done by one circuit: rippleAdd, the “ripple carry adder”
- We will proceed in stages
 - Adding two bits: halfAdd
 - Adding three bits: fullAdd
 - Adding two integers: rippleAdd
 - Subtracting an integer from another
- Multiplication and division are more complicated
 - Not too complicated, but we won't do them in this course

Review: binary addition


- You can add two binary numbers x and y the same way as decimal numbers
- Write one number above the other
- Work through each column, from right to left
- In each column, add the bit from x , the bit from y , and the carry from the column to the right
- This gives the sum bit s for the column, and the carry output which goes to the left
- In each column we add three bits: a carry input, a bit from x , and a bit from y

The half adder: adding two bits

- A half adder adds two bits
 - Since the result could be 0, 1, or 2, we need a two-bit representation of the sum, called (carry, sum)
- Specify the circuit abstractly by writing the complete addition table
 - Then we recognise that the carry function is just `and2`, and the sum function is just `xor2`

x	y	result	carry	sum
0	0	0	0	0
0	1	1	0	1
1	0	1	0	1
1	1	2	1	0

The half adder

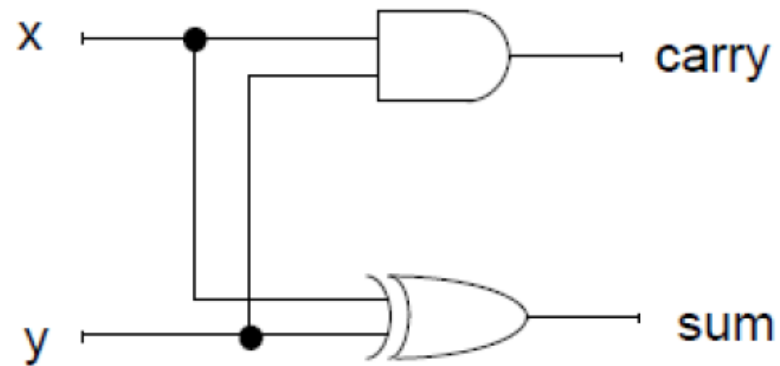

x	y	result	carry	sum
0	0	0	0	0
0	1	1	0	1
1	0	1	0	1
1	1	2	1	0

The full adder: adding three bits


- To add two binary numbers, we must add **three** bits for each column
 - The two data bits (one from each word)
 - The carry input from the column to the left
- **Solution:** the **full adder**
- A full adder adds three bits x , y , z and outputs a carry c and sum s

Truth table of full adder

x	y	z	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- The **sum is 1** if an odd number of inputs are 1
- The **carry is 1** if two or more inputs are 1
- You can view **c** and **s** as a 2-bit binary number giving the result

The full adder circuit

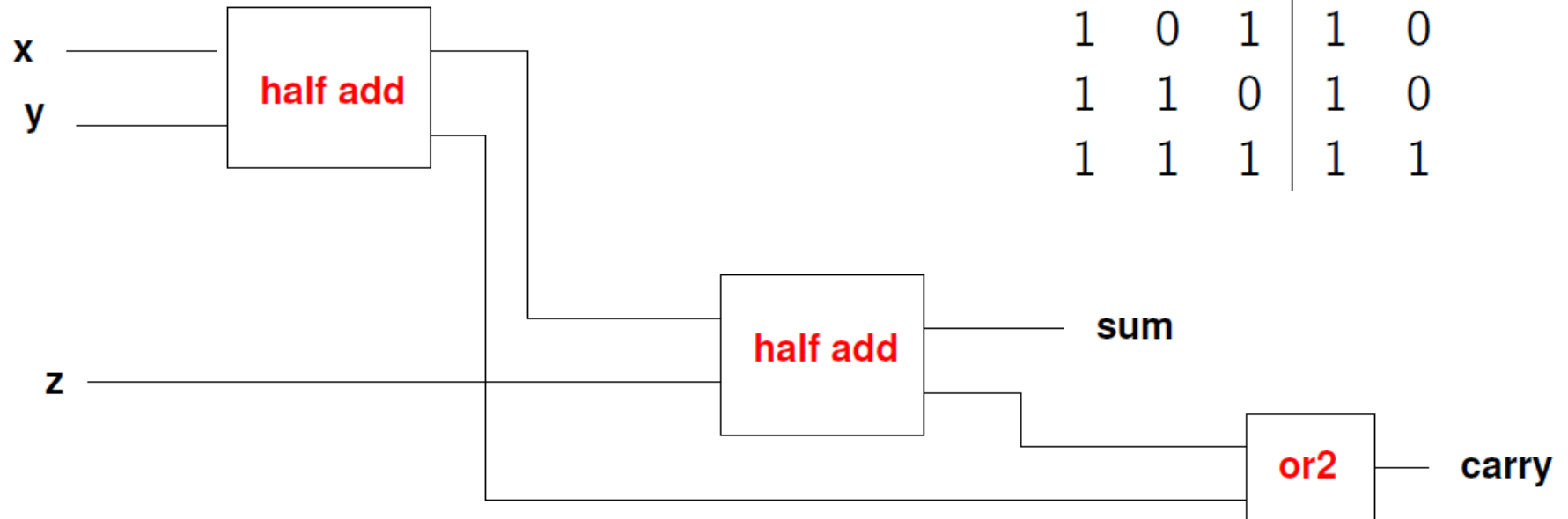

x	y	z	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Binary word addition

- Use a full adder circuit for each bit position
- To add two 16-bit words x and y , we have 16 separate full adders
- Each full adder receives
 - A bit from x and a bit from y
 - The carry output from the full adder to the right


Add the weight 4 column (from Lecture 2)

- In the middle of an addition

		128	64	32	16	8	4	2	1
c						1	0	0	0
x		0	0	1	0	1	1	0	1
y		0	1	0	0	1	1	1	0
s							0	1	1

- A full adder will calculate the carry and sum in every column

4-Bit Ripple Carry Adder

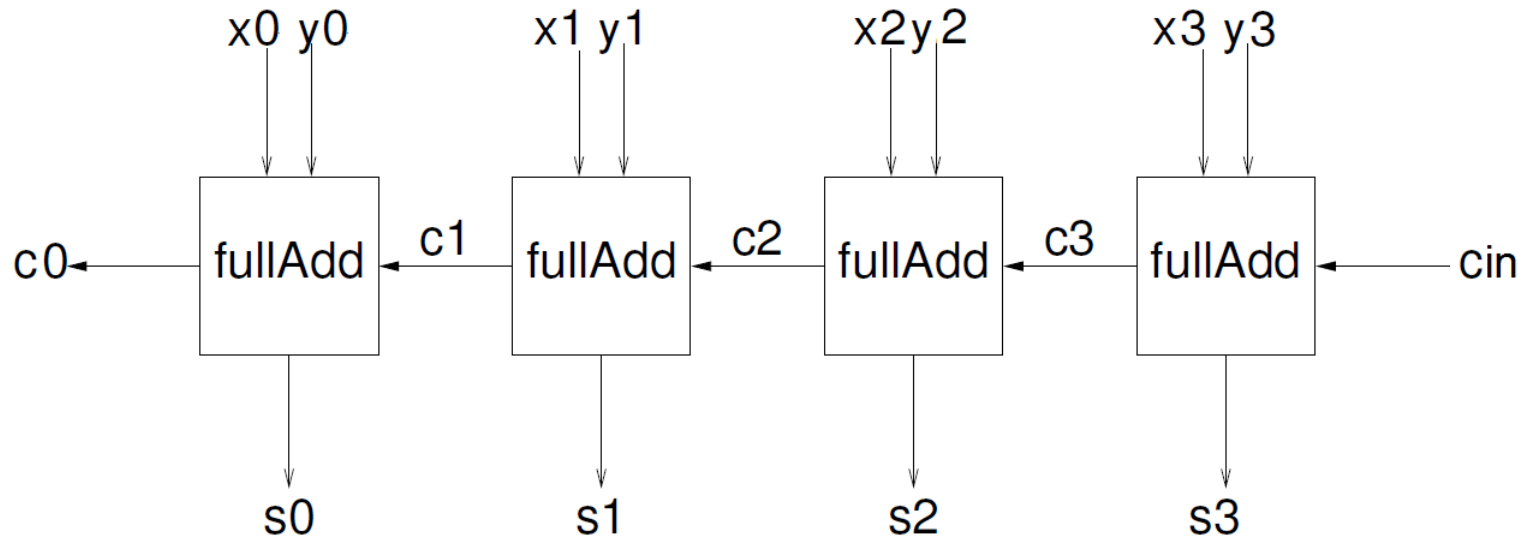

- **Inputs:** word x , word y , carry input bit c
- **Outputs:** sum s , carry output
- Each bit position receives a bit from x , a bit from y , and a carry input from the position to the right
- A full adder circuit adds these three bits

Pascal's adder



- Carry propagation using gears!
- Designed by the French philosopher and mathematician (and early computer scientist!) Blaise Pascal (1623-1662)

Subtraction

- Work with two's complement numbers
- Note that $x - y = x + (-y)$
- Recall that to negate a number, you invert the bits and add 1
- To invert the bits of y , just put an inverter on each bit of y
- To add 1, just set the carry input to the entire ripple carry adder to 1
- **So:** use a ripple carry adder, with each bit of y inverted, and with carry input = 1, and the output will be $x - y$
- Modern computers use the adder circuit to perform subtraction and addition

Outline

- Boolean algebra
- Addition and subtraction
 - Half adder
 - Full adder
 - Ripple carry adder
 - Subtraction
- Circuit simulation


Circuit simulation

- After designing a circuit, **how do we find out whether it works?**
- **One way:** build the circuit out of transistors, and test it
- To fabricate a design on a chip takes a long time and costs a lot of money
- **Better way:** use a **circuit simulator**

Software tools for circuit design

- “Real world” hardware is designed using special languages called **computer hardware description languages**
- An easier approach (though less powerful) is to use a **schematic capture** application
 - You draw the circuit interactively
 - A diagram of a circuit is called a **schematic diagram**
 - The software then simulates it
- We will use a schematic capture and simulation tool called **LogicWorks**


A schematic diagram in LogicSim

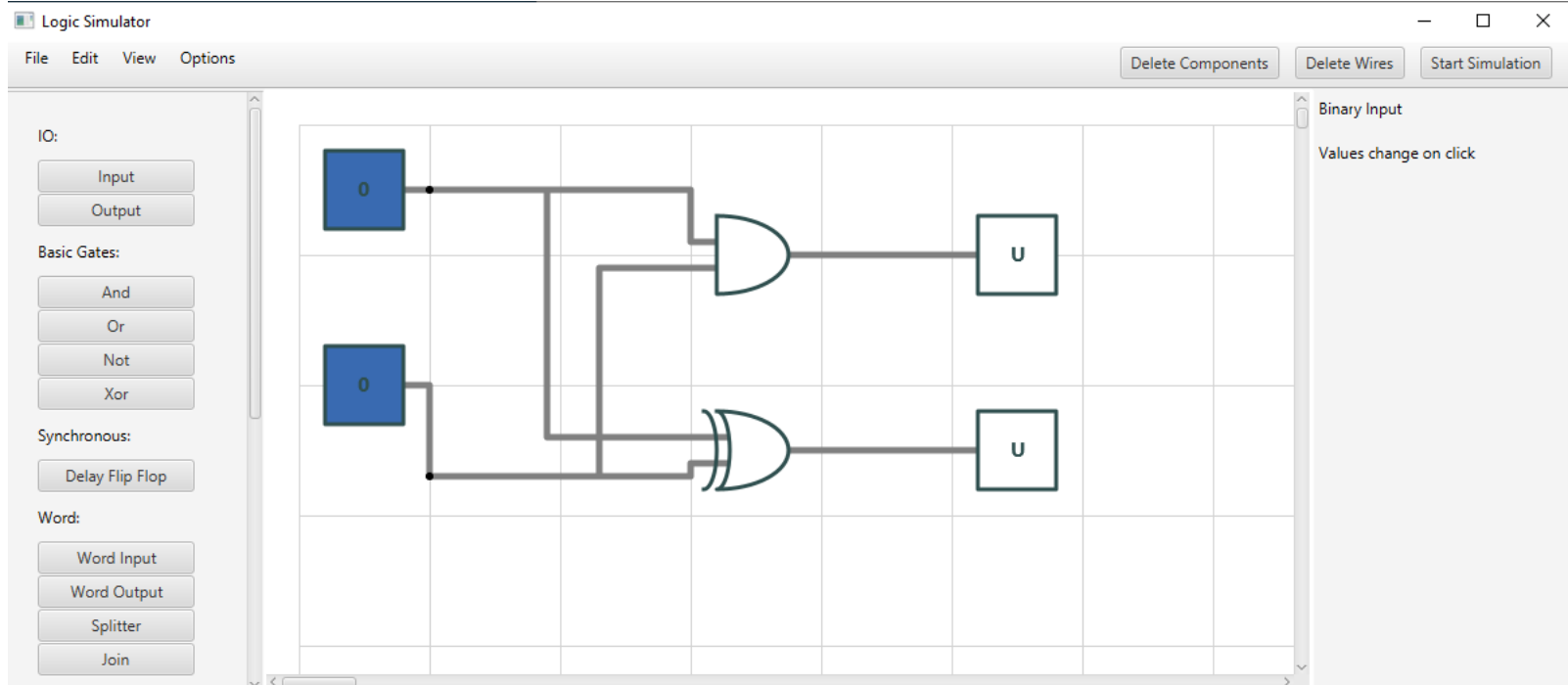

Drawing a circuit

- Some basic points
 - Select a component from combo box in the lower right
 - You'll see the component in a little window on upper right
 - Click it, and drag to where you want to place the component
 - To draw a wire, click the + icon on toolbar
 - For input, use a binary switch
 - For output, use a binary probe
- See document on Moodle for more about how to use LogicWorks

Half adder circuit: inputs $x=0$, $y=0$

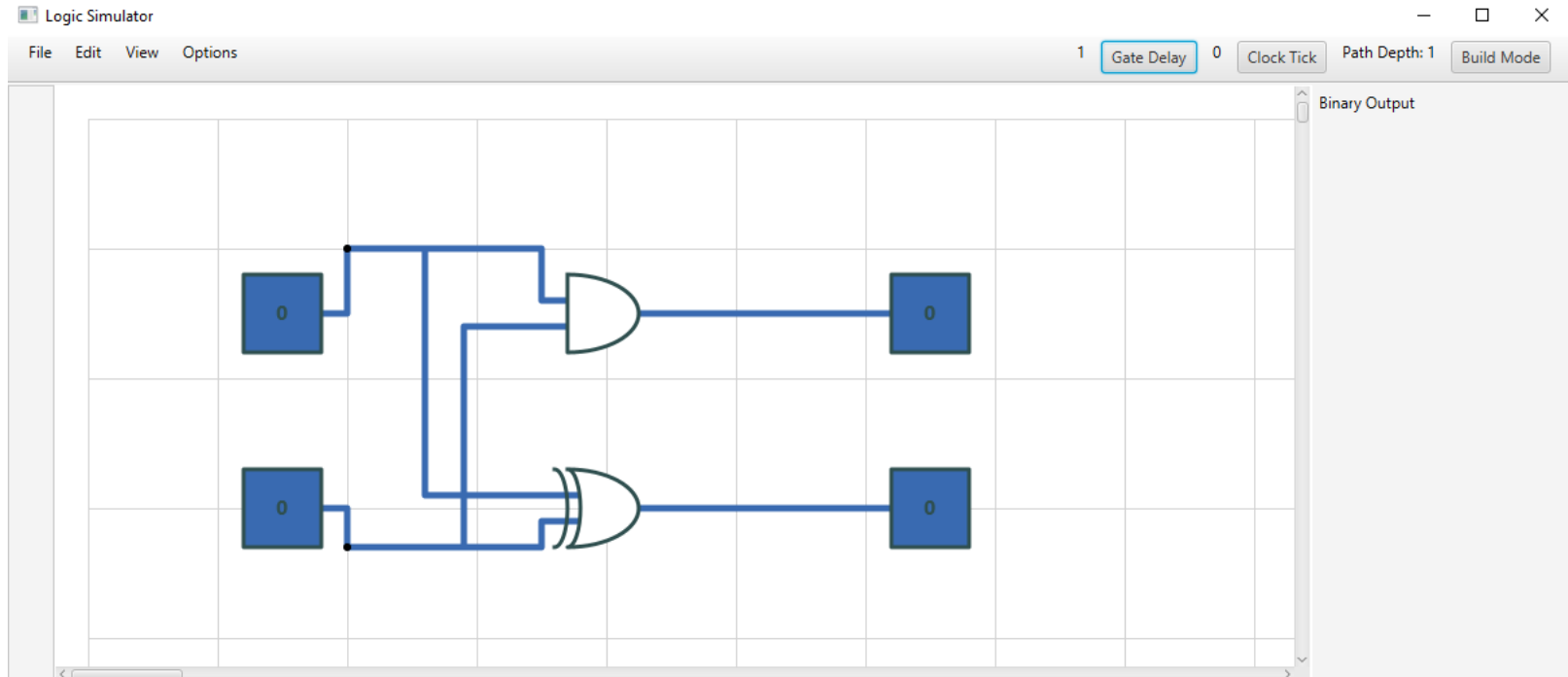


Aim: find out whether the circuit works


- The circuit has to give the correct outputs for every possible values of the inputs
- So there are four separate simulation problems
- For each line, set x and y using the switches, and record the outputs c and s in the table

x	y	c	s
0	0	?	?
0	1	?	?
1	0	?	?
1	1	?	?


Half adder circuit: inputs $x=0$, $y=1$

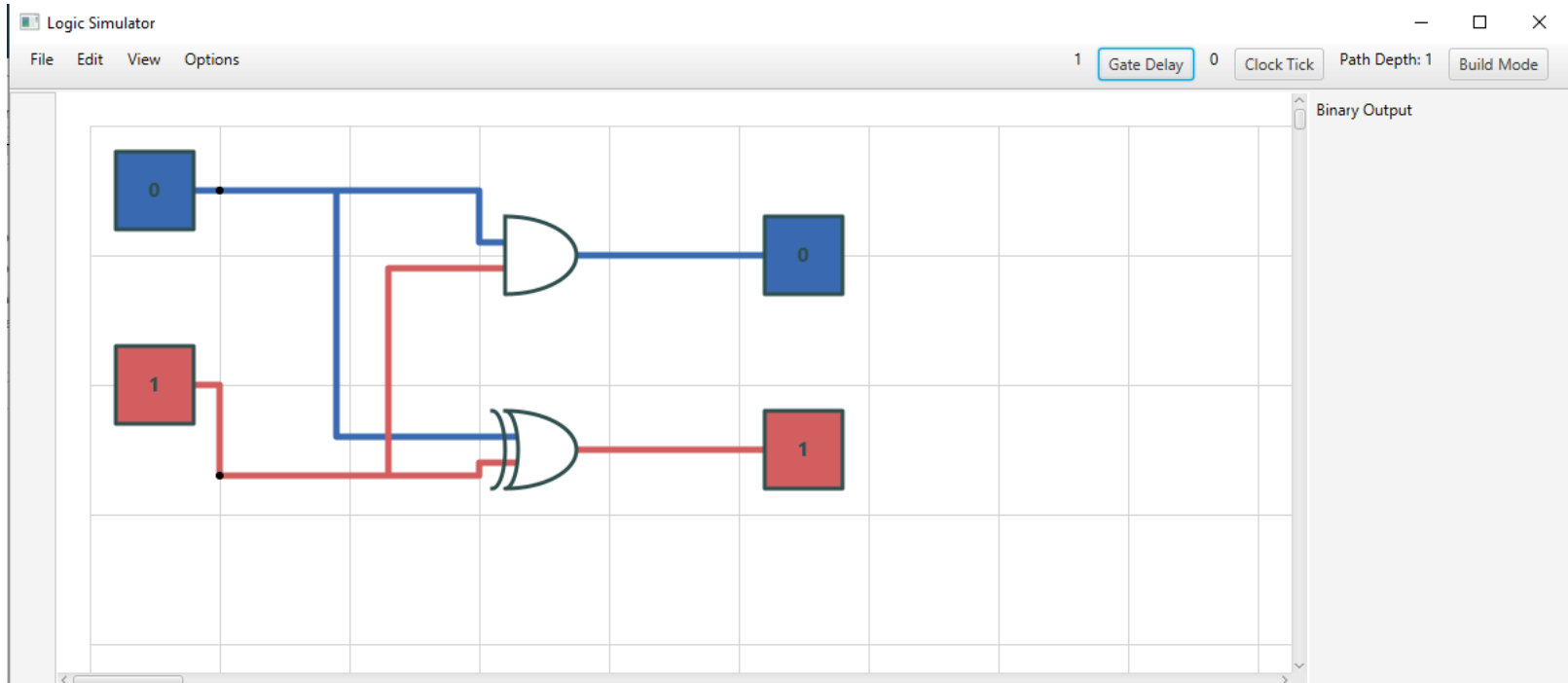

Half adder circuit: inputs $x=1$, $y=0$

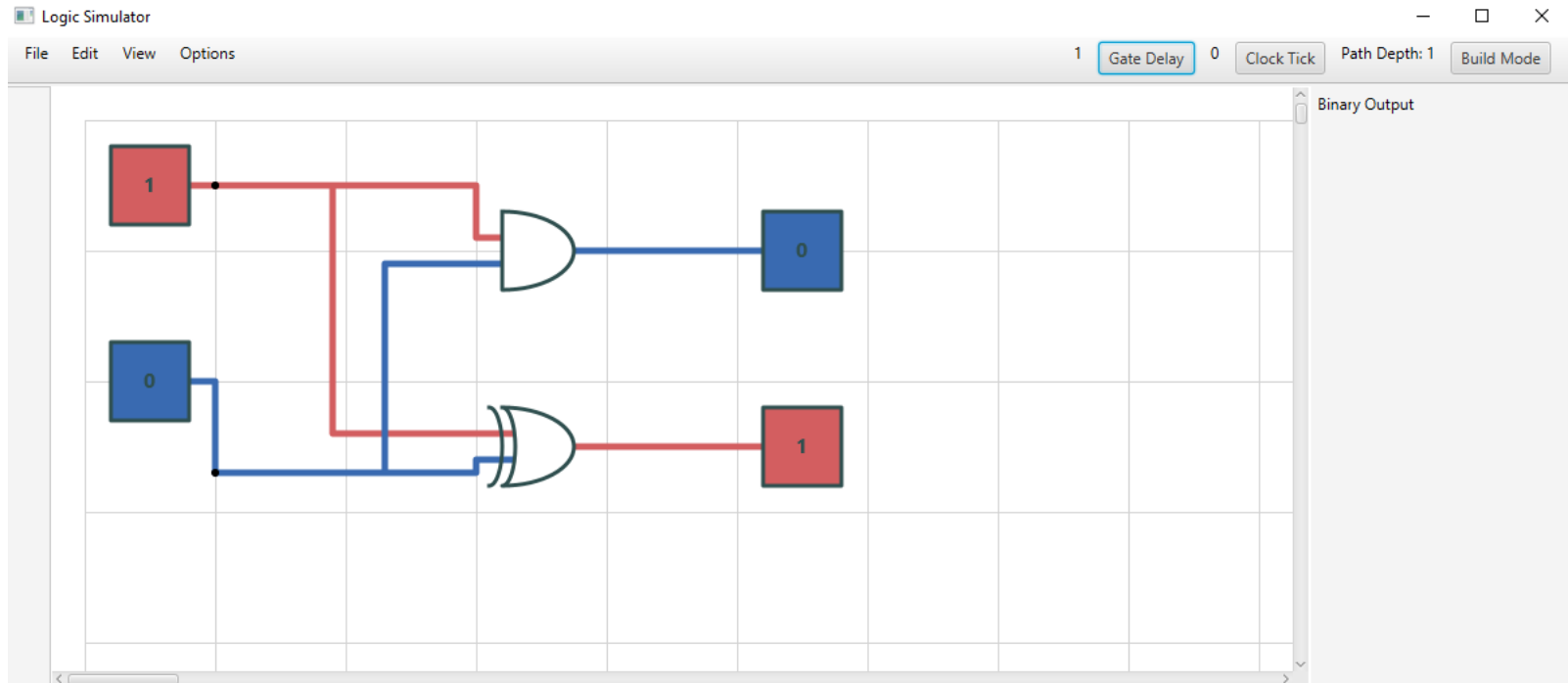

Half adder circuit: inputs $x=1$, $y=1$

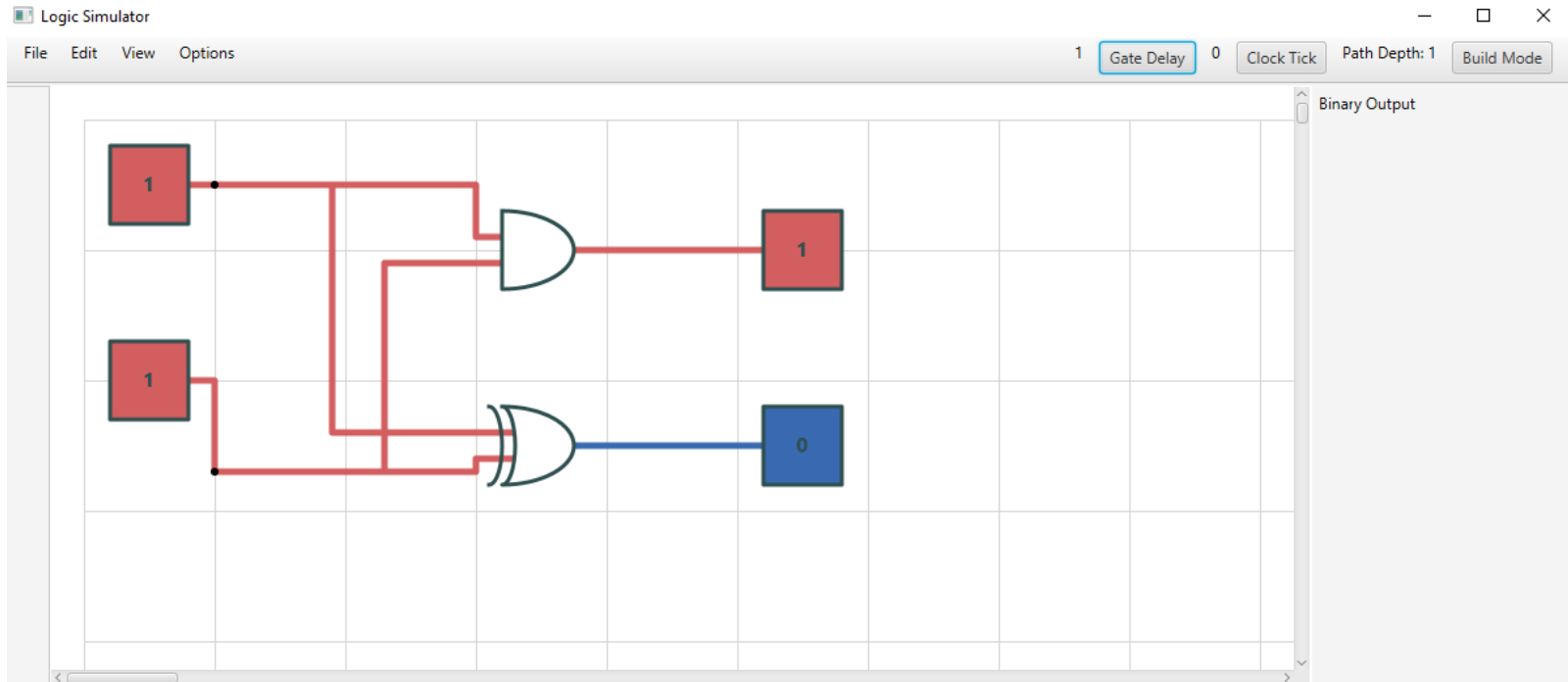

Record simulation results in a truth table

- For each row, set the input switches for x , y , observe the outputs c , s and fill in the truth table

x	y	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- The table gives the correct carry and sum outputs, so the circuit works correctly

To do

- Revise the lecture slides
- Finish Quiz 1 by Friday night
- Quiz 2 available
- Check the solutions to Week 2 Lab (on Moodle, at the weekend)
- Always read the solutions, even if you know the answer
 - Sometimes the model solution will give additional information
- Study the ripple carry adder circuit
 - Understand how it's doing the same thing you do when you add numbers by hand, with carry where needed



<https://xkcd.com/302/>